

LAB 9-10 – NANO PROCESSOR DESIGN COMPETITION

DEPT. OF COMPUTER SCIENCE AND ENGINEERING, UNIVERSITY OF MORATUWA

**Participants - SENARATNE R.R.S.N. 210592C,
SENEVIRATHNE R.J.M. 210598B**

Lab Task –

We had to design a 4-bit Nano processor capable of executing 4 instructions. To build this circuit, we needed to develop the components that we have built in the previous labs.

- 1) Designed and developed a 4-bit arithmetic unit that can add/subtract signed integers.**
- 2) Designed and developed MUXs (2-way 3-bit, 2-way 4-bit, 8-way 4-bit)**
- 3) Designed a register bank with 8 registers.**
- 4) Designed a program counter and a 3-bit adder which can increment program counter to get the desired register address.**
- 5) Designed and build the processor capable of executing 4 instructions (MOVI, ADD, NEG, JZR) that are stored in ROM.**

- 6) Decoded instructions to activate necessary components on the processor.**
- 7) Write the assembly program to calculate the total of all integers between 1 and 3. Converted the assembly code to machine code and hard code it and stored to ROM. Demonstrate the result using BASYS 3 board.**

Contribution –

**210598B – 4- bit Adder/Subtractor
Program Rom
3 – bit Adder
Rom
3-bit PC**

(15 hours spent)

**210592C – 2 way 3-bit MUX
2 way 4-bit MUX
8way 4-bit MUX
3 – bit Program Counter
Register Bank
Instruction Decoder**

(15 hours spent)

There are some modifications of Adders, Rom.

Simulation test bench files are submitted separately as a zip file.

Instructions in machine code

```
101110000001
100010000010
100100000011
001110010000
001110100000
101110000001
110000000000
000000000000
000000000000
```

Assembly program

```
MOVI R7,1    ; R7 <- 1
MOVI R1,2    ; R2 <- 2
MOVI R2,3    ; R2 <- 3
ADD R7       ; R7 <- R7 + R1
ADD R7       ; R7 <- R7 + R2
JZR R0,0     ; IF R0 = 0 JUMP TO LINE 0
```

4-bit Adder/Subtractor

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Adder_Subtractor_4bit is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0); --input A
          B : in STD_LOGIC_VECTOR (3 downto 0); --input B
          M : in STD_LOGIC;                    -- Adder Subtractor switch
          S : out STD_LOGIC_VECTOR (3 downto 0);--Output
          C_OUT : out STD_LOGIC;                --Carry or Borrow out
          OVERFLOW: out STD_LOGIC;              --Overflow Flag
          ZERO: out STD_LOGIC                   --Zero Flag
        );
end Adder_Subtractor_4bit;

architecture Behavioral of Adder_Subtractor_4bit is
    component FA
        port (
            A: in std_logic;
            B: in std_logic;
            C_in: in std_logic;
            S: out std_logic;
            C_out: out std_logic);
        end component;

    SIGNAL FA0_C, FA1_C, FA2_C, FA3_C,CARRY: std_logic;
    SIGNAL B_temp:STD_LOGIC_VECTOR (3 downto 0);
    SIGNAL S_temp:STD_LOGIC_VECTOR (3 downto 0);
begin

    FA_0 : FA
        port map (
            A => A(0),
            B => B_temp(0),
            C_in => M ,
            S => S_temp(0),
            C_out => FA0_C);

    FA_1 : FA
        port map (
            A => A(1),
```

```

        B => B_temp(1),
        C_in => FA0_C,
        S => S_temp(1),
        C_out => FA1_C);

FA_2 : FA
    port map (
        A => A(2),
        B => B_temp(2),
        C_in => FA1_C,
        S => S_temp(2),
        C_out => FA2_C);

FA_3 : FA
    port map (
        A => A(3),
        B => B_temp(3),
        C_in => FA2_C,
        S => S_temp(3),
        C_out => CARRY);

B_temp(0)<=B(0) XOR M;
B_temp(1)<=B(1) XOR M;
B_temp(2)<=B(2) XOR M;
B_temp(3)<=B(3) XOR M;

C_OUT<=CARRY;
S<=S_temp;

ZERO <=NOT S_temp(0) AND NOT S_temp(1) AND NOT S_temp(2) AND NOT
S_temp(3) AND CARRY;

OVERFLOW<= M AND NOT(FA2_C AND (A(3) XOR B_temp(3)));

end Behavioral;

```

3 – bit Adder

```

-- Company:
-- Engineer:
--
-- Create Date: 06/04/2023 12:38:53 AM
-- Design Name:
-- Module Name: Adder_3bit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:

```

```
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;
```

```
entity Adder_3bit is  
  Port ( A : in STD_LOGIC_VECTOR (2 downto 0);  
        S : out STD_LOGIC_VECTOR (2 downto 0));  
end Adder_3bit;
```

```
architecture Behavioral of Adder_3bit is
```

```
  component FA  
    port (  
      A: in std_logic;  
      B: in std_logic;  
      C_in: in std_logic;  
      S: out std_logic;  
      C_out: out std_logic);  
  end component;
```

```
  SIGNAL FA0_S, FA0_C, FA1_S, FA1_C, FA2_S, FA2_C, C : std_logic;
```

```
begin  
  FA_0 : FA  
    port map (  
      A => A(0),  
      B => '1',  
      C_in => '0',  
      S => S(0),  
      C_Out => FA0_C);  
  FA_1 : FA  
    port map (  
      A => A(1),  
      B => '0',  
      C_in => FA0_C,  
      S => S(1),  
      C_Out => FA1_C);
```

```

FA_2 : FA
  port map (
    A => A(2),
    B => '0',
    C_in => FA1_C,
    S => S(2),
    C_Out => C);
end Behavioral;

```

Program Rom

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity ROM is
  Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
        data : out STD_LOGIC_VECTOR (11 downto 0));
end ROM;

architecture Behavioral of ROM is

  type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);
  signal rom : rom_type :=(
    "101110000001", --0   MOVI R7,1
    "100010000010", --1   MOVI R1,2
    "100100000001", --2   MOVI R2,3
    "001110010000", --3   ADD R7 <- R7 + R1
    "001110100000", --4   ADD R7 <- R7 + R2
    "110000000000", --5   JZR R0,0
    "000000000000", --6
    "000000000000" --7
  );
begin
  data <= rom(to_integer(unsigned(address)));
end Behavioral;

```

3 – bit Program Counter

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity ProgramCounter is
    Port ( Reset : in STD_LOGIC;           --Reset Button
          Clk : in STD_LOGIC;             --Clock
          A : in STD_LOGIC_VECTOR (2 downto 0); --ProgramCounter_in
          memory_select : out STD_LOGIC_VECTOR (2 downto 0)); ----
    ProgramCounter_select Address
end ProgramCounter;

architecture Behavioral of ProgramCounter is
begin
    process(Clk)
    begin
        if(rising_edge(Clk)) then
            if(Reset='1') then
                memory_select<="000";
            else
                memory_select<=A;
            end if;
        end if;
    end process;
end Behavioral;

```

MUX_2way_3-bit

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 06/09/2023 10:20:28 AM
-- Design Name:
-- Module Name: MUX_2_3bit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--

```


-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity MUX_2_3bit is
 Port (A : in STD_LOGIC_VECTOR (2 downto 0);
 B: in STD_LOGIC_VECTOR (2 downto 0);
 S : in STD_LOGIC;
 Q : out STD_LOGIC_VECTOR (2 downto 0));
end MUX_2_3bit;

architecture Behavioral of MUX_2_3bit is

begin
 process (S,A,B)
 begin
 if S='0' then
 Q <= B;
 else
 Q<= A ;
 end if;
 end process;
end Behavioral;

MUX_2way_4-bit

-- Company:
-- Engineer:
--
-- Create Date: 06/09/2023 10:18:45 AM
-- Design Name:
-- Module Name: MUX_2_4bit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:

```
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity MUX_2_4bit is
  Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
        B : in STD_LOGIC_VECTOR (3 downto 0);
        Q : out STD_LOGIC_VECTOR (3 downto 0);
        S : in STD_LOGIC);
end MUX_2_4bit;
```

```
architecture Behavioral of MUX_2_4bit is
```

```
  signal ls_s : std_logic;
  signal asu_s : std_logic_vector(3 downto 0);
  signal immVal_s : std_logic_vector(3 downto 0);
  signal output : std_logic_vector(3 downto 0);
begin
```

```
  ls_s <= S;
  asu_s <= B;
  immVal_s <= A;
  process (ls_s, asu_s, immVal_s) begin
    if ls_s='1' then
      output<=asu_s;
    else
      output<=immVal_s;
    end if;
  end process;
```

```
  Q <= output;
end Behavioral;
```

MUX_8way_4-bit

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 06/09/2023 10:16:43 AM  
-- Design Name:  
-- Module Name: MUX_8_4bit - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;
```

```
entity MUX_8_4bit is  
  Port ( Reg_Sel : in STD_LOGIC_VECTOR (2 downto 0);  
        R0 : in STD_LOGIC_VECTOR (3 downto 0);  
        R1 : in STD_LOGIC_VECTOR (3 downto 0);  
        R2 : in STD_LOGIC_VECTOR (3 downto 0);  
        R3 : in STD_LOGIC_VECTOR (3 downto 0);  
        R4 : in STD_LOGIC_VECTOR (3 downto 0);  
        R5 : in STD_LOGIC_VECTOR (3 downto 0);  
        R6 : in STD_LOGIC_VECTOR (3 downto 0);  
        R7 : in STD_LOGIC_VECTOR (3 downto 0);  
        Mux_Out : out STD_LOGIC_VECTOR (3 downto 0));  
end MUX_8_4bit;
```

architecture Behavioral of MUX_8_4bit is

component Decoder_3_to_8

port(I : in STD_LOGIC_VECTOR (2 downto 0);

EN : in STD_LOGIC;

Y : out STD_LOGIC_VECTOR (7 downto 0));

end component;

signal Decoder_Out : std_logic_vector(7 downto 0);

signal Mux_Output : std_logic_vector(3 downto 0);

signal D0 : std_logic_vector(3 downto 0);

signal A0 : std_logic_vector(3 downto 0);

signal D1 : std_logic_vector(3 downto 0);

signal A1 : std_logic_vector(3 downto 0);

signal D2 : std_logic_vector(3 downto 0);

signal A2 : std_logic_vector(3 downto 0);

signal D3 : std_logic_vector(3 downto 0);

signal A3 : std_logic_vector(3 downto 0);

signal D4 : std_logic_vector(3 downto 0);

signal A4 : std_logic_vector(3 downto 0);

signal D5 : std_logic_vector(3 downto 0);

signal A5 : std_logic_vector(3 downto 0);

signal D6 : std_logic_vector(3 downto 0);

signal A6 : std_logic_vector(3 downto 0);

signal D7 : std_logic_vector(3 downto 0);

signal A7 : std_logic_vector(3 downto 0);

begin

Decoder_3_to_8_0 : Decoder_3_to_8

port map (

I => Reg_Sel,

EN => '1',

Y => Decoder_Out

);

D0 <= R0 AND A0;

D1 <= R1 AND A1;

D2 <= R2 AND A2;

D3 <= R3 AND A3;

D4 <= R4 AND A4;

D5 <= R5 AND A5;

D6 <= R6 AND A6;

D7 <= R7 AND A7;

A0 <= (others=> Decoder_Out(0));

A1 <= (others=> Decoder_Out(1));

A2 <= (others=> Decoder_Out(2));

A3 <= (others=> Decoder_Out(3));

A4 <= (others=> Decoder_Out(4));

A5 <= (others=> Decoder_Out(5));

A6 <= (others=> Decoder_Out(6));

A7 <= (others=> Decoder_Out(7));

Mux_Out <= D0 or D1 or D2 or D3 or D4 or D5 or D6 or D7;

end Behavioral;

Register Bank

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 06/09/2023 09:58:59 AM  
-- Design Name:  
-- Module Name: Register_Bank - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----
```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Reg_Bank is
 Port (Clk : in STD_LOGIC;
 Reg_EN : in STD_LOGIC_VECTOR (2 downto 0);
 Reset :in STD_LOGIC;
 Reg_Bank_In : in STD_LOGIC_VECTOR (3 downto 0);
 REG_0_OUT : out STD_LOGIC_VECTOR (3 downto 0);
 REG_1_OUT : out STD_LOGIC_VECTOR (3 downto 0);
 REG_2_OUT : out STD_LOGIC_VECTOR (3 downto 0);
 REG_3_OUT : out STD_LOGIC_VECTOR (3 downto 0);
 REG_4_OUT : out STD_LOGIC_VECTOR (3 downto 0);
 REG_5_OUT : out STD_LOGIC_VECTOR (3 downto 0);

```

        REG_6_OUT : out STD_LOGIC_VECTOR (3 downto 0);
        REG_7_OUT : out STD_LOGIC_VECTOR (3 downto 0));
end Reg_Bank;

```

architecture Behavioral of Reg_Bank is

component REG

```

    port(
        D : in STD_LOGIC_VECTOR (3 downto 0);
        En : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Reset :in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (3 downto 0)
    );
end component;

```

component Decoder_3_to_8

```

    Port (
        I : in STD_LOGIC_VECTOR (2 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC_VECTOR (7 downto 0)
    );
end component;

```

```

signal decoder_out : std_LOGIC_VECTOR(7 downto 0);

```

begin

Reg_Bank_Decoder : Decoder_3_to_8

```

    port map(
        I => Reg_EN,
        EN => '1',
        Y => decoder_out
    );

```

REG_0 : REG

```

    port map(
        D => "0000",
        EN=> decoder_out(0),
        Clk => Clk,
        Reset=>Reset,
        Q=> REG_0_OUT
    );

```

REG_1 : REG

```

    port map(
        D => Reg_Bank_In,
        EN=> decoder_out(1),
        Clk => Clk,
        Reset=>Reset,
        Q=> REG_1_OUT
    );

```

REG_2 : REG

```

    port map(
        D => Reg_Bank_In,

```

```

        EN=> decoder_out(2),
        Clk => Clk,
        Reset=>Reset,
        Q=> REG_2_OUT
    );
REG_3 : REG
    port map(
        D => Reg_Bank_In,
        EN=> decoder_out(3),
        Clk => Clk,
        Reset=>Reset,
        Q=> REG_3_OUT
    );
REG_4 : REG
    port map(
        D => Reg_Bank_In,
        EN=> decoder_out(4),
        Clk => Clk,
        Reset=>Reset,
        Q=> REG_4_OUT
    );
REG_5 : REG
    port map(
        D => Reg_Bank_In,
        EN=> decoder_out(5),
        Clk => Clk,
        Reset=>Reset,
        Q=> REG_5_OUT
    );
REG_6 : REG
    port map(
        D => Reg_Bank_In,
        EN=> decoder_out(6),
        Clk => Clk,
        Reset=>Reset,
        Q=> REG_6_OUT
    );
REG_7 : REG
    port map(
        D =>Reg_Bank_In,
        EN=> decoder_out(7),
        Clk => Clk,
        Reset=>Reset,
        Q=> REG_7_OUT
    );

end Behavioral;

```

Instruction Decoder

```

-- Company:
-- Engineer:
--
-- Create Date: 06/09/2023 10:21:32 AM
-- Design Name:
-- Module Name: InstructionDecorder - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity InstructionDecoder is

```

```

    Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0); --Instruction
          RCJ : in STD_LOGIC_VECTOR (3 downto 0);          --Register check for jump
          RegEn : out STD_LOGIC_VECTOR (2 downto 0);        --Register Enable
          LS : out STD_LOGIC;                                --Load Select
          Immediatevalue : out STD_LOGIC_VECTOR (3 downto 0);--Immediate Value
          Reg_1 : out STD_LOGIC_VECTOR (2 downto 0);        --Register Select 1
          Reg_2 : out STD_LOGIC_VECTOR (2 downto 0);        --Register Select 2
          Add_Sub_Select : out STD_LOGIC;                    --Add_Sub_Select
          JumpFlag : out STD_LOGIC;                          --Jump Flag
          ATJ : out STD_LOGIC_VECTOR (2 downto 0));          --Address to jump
end InstructionDecoder;

```

```

architecture Behavioral of InstructionDecoder is

```

```

    SIGNAL regEn_temp : std_logic_vector(2 downto 0);
    SIGNAL regChkForJump : std_logic_vector(3 downto 0);
    SIGNAL reg_select_temp_1 : std_logic_vector(2 downto 0);
    SIGNAL op : std_logic_vector(1 downto 0);
    SIGNAL reg_1_temp : std_logic_vector(2 downto 0);

```



```

SIGNAL reg_2_temp : std_logic_vector(2 downto 0);
SIGNAL immediateValue_temp : std_logic_vector(3 downto 0);
SIGNAL jumpAddress : std_logic_vector(2 downto 0);
SIGNAL reg_select_temp_2 : std_logic_vector(2 downto 0);
SIGNAL LS_temp : std_logic;
SIGNAL addSub_temp : std_logic;
SIGNAL immVal_temp : std_logic_vector(3 downto 0);

SIGNAL jumpSel : std_logic := '0';
begin
    op <= Instruction(11 downto 10);
    reg_1_temp <= Instruction(9 downto 7);
    reg_2_temp <= Instruction(6 downto 4);
    immediateValue_temp <= Instruction(3 downto 0);
    process (op, reg_1_temp, reg_2_temp, immediateValue_temp)

begin
    jumpSel <= '0';
    if op = "00" then
        reg_select_temp_1 <= reg_1_temp;
        reg_select_temp_2 <= reg_2_temp;
        addSub_temp <= '0';
        LS_temp <= '1';
        regEn_temp <= reg_1_temp;
    elsif op = "01" then
        reg_select_temp_1 <= reg_1_temp;
        reg_select_temp_2 <= "000";

        addSub_temp <= '1';
        LS_temp <= '1';
        regEn_temp <= reg_1_temp;
    elsif op = "10" then

        immVal_temp <= immediateValue_temp;
        LS_temp <= '0';
        regEn_temp <= reg_1_temp;
    elsif op = "11" then
        reg_select_temp_1 <= reg_1_temp;
        jumpAddress <= immediateValue_temp(2 downto 0);
        if regChkForJump = "0000" then
            jumpSel <= '1';
        else
            jumpSel <= '0';
        end if;
    end if;
end process;

JumpFlag <= jumpSel;
regChkForJump <= RCJ;
RegEn <= regEn_temp;
LS <= LS_temp;
Immediatevalue <= immVal_temp;
Reg_1 <= reg_select_temp_1;

```

```

    Reg_2 <= reg_select_temp_2;
    Add_Sub_Select <= addSub_temp;
    ATJ <= jumpAddress;
end Behavioral;

```

Nano Processor

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 06/09/2023 10:25:44 AM
-- Design Name:
-- Module Name: nano_processor - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity nano_processor is
    Port ( pushButton : in STD_LOGIC;
          Imm_Value:out std_logic_vector(3 downto 0);
          Clk : in STD_LOGIC;
          nextInsVal : out std_logic_vector(2 downto 0);
          RegisterEnable:out std_logic_vector(2 downto 0);
          RegisterBank_DataIn: out std_logic_vector(3 downto 0);

```

```

        LED : out STD_LOGIC_VECTOR (3 downto 0);
        LED_R6 : out std_logic_vector(3 downto 0);
        LED_R5 : out std_logic_vector(3 downto 0);
        LED_OVERFLOW:out STD_LOGIC;
        LED_ZERO:out STD_LOGIC;
        Instruction_temp : out std_logic_vector(11 downto 0)

    );
end nano_processor;

architecture Behavioral of nano_processor is
    COMPONENT Slow_Clk is
        Port ( Clk_in : in STD_LOGIC;
              Clk_out : out STD_LOGIC);
    end COMPONENT;

--Instruction Decoder
    COMPONENT InstructionDecoder is
        Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
              RCJ : in STD_LOGIC_VECTOR (3 downto 0);
              RegEn : out STD_LOGIC_VECTOR (2 downto 0);
              LS : out STD_LOGIC;
              Immediatevalue : out STD_LOGIC_VECTOR (3 downto 0);
              Reg_1 : out STD_LOGIC_VECTOR (2 downto 0);
              Reg_2 : out STD_LOGIC_VECTOR (2 downto 0);
              Add_Sub_Select : out STD_LOGIC;
              JumpFlag : out STD_LOGIC;
              ATJ : out STD_LOGIC_VECTOR (2 downto 0));
    end COMPONENT;

--ROM
    COMPONENT ROM is
        Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
              data : out STD_LOGIC_VECTOR (11 downto 0));
    end COMPONENT;

--Adder 3bit
    COMPONENT Adder_3bit is
        Port ( A : in STD_LOGIC_VECTOR(2 DOWNTO 0);
              B : in STD_LOGIC_VECTOR(2 DOWNTO 0);
              S : out STD_LOGIC_VECTOR(2 DOWNTO 0);
              C_out : out STD_LOGIC);
    END COMPONENT ;

--MUX 2 3bit
    COMPONENT MUX_2_3bit is
        Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
              B: in STD_LOGIC_VECTOR (2 downto 0);
              S : in STD_LOGIC;
              Q : out STD_LOGIC_VECTOR (2 downto 0));

```

end COMPONENT;

--Program Counter

COMPONENT ProgramCounter is

Port (Reset : in STD_LOGIC;

Clk : in STD_LOGIC;

A : in STD_LOGIC_VECTOR (2 downto 0);

memory_select : out STD_LOGIC_VECTOR (2 downto 0));

end COMPONENT;

--Register Bank

COMPONENT Reg_Bank is

Port (Clk : in STD_LOGIC;

Reg_EN : in STD_LOGIC_VECTOR (2 downto 0);

Reset : in STD_LOGIC;

Reg_Bank_In : in STD_LOGIC_VECTOR (3 downto 0);

REG_0_OUT : out STD_LOGIC_VECTOR (3 downto 0);

REG_1_OUT : out STD_LOGIC_VECTOR (3 downto 0);

REG_2_OUT : out STD_LOGIC_VECTOR (3 downto 0);

REG_3_OUT : out STD_LOGIC_VECTOR (3 downto 0);

REG_4_OUT : out STD_LOGIC_VECTOR (3 downto 0);

REG_5_OUT : out STD_LOGIC_VECTOR (3 downto 0);

REG_6_OUT : out STD_LOGIC_VECTOR (3 downto 0);

REG_7_OUT : out STD_LOGIC_VECTOR (3 downto 0));

end COMPONENT;

--MUX 8 4bit

COMPONENT MUX_8_4bit is

Port (Reg_Sel : in STD_LOGIC_VECTOR (2 downto 0);

R0 : in STD_LOGIC_VECTOR (3 downto 0);

R1 : in STD_LOGIC_VECTOR (3 downto 0);

R2 : in STD_LOGIC_VECTOR (3 downto 0);

R3 : in STD_LOGIC_VECTOR (3 downto 0);

R4 : in STD_LOGIC_VECTOR (3 downto 0);

R5 : in STD_LOGIC_VECTOR (3 downto 0);

R6 : in STD_LOGIC_VECTOR (3 downto 0);

R7 : in STD_LOGIC_VECTOR (3 downto 0);

Mux_Out : out STD_LOGIC_VECTOR (3 downto 0));

end COMPONENT;

--MUX 2 4bit

COMPONENT MUX_2_4bit is

Port (A : in STD_LOGIC_VECTOR (3 downto 0);

B : in STD_LOGIC_VECTOR (3 downto 0);

S : in STD_LOGIC;

Q : out STD_LOGIC_VECTOR (3 downto 0));

end COMPONENT;

--Adder_Subtractor 4bit

COMPONENT Adder_Subtractor_4bit IS

Port (A : in STD_LOGIC_VECTOR (3 downto 0);

```

        B : in STD_LOGIC_VECTOR (3 downto 0);
        M : in STD_LOGIC;
        S : out STD_LOGIC_VECTOR (3 downto 0);
        C_OUT : out STD_LOGIC;
        OVERFLOW: out STD_LOGIC;
        ZERO: out STD_LOGIC );
end COMPONENT;

SIGNAL clk_temp:STD_LOGIC;
SIGNAL clk_temp2:STD_LOGIC;

---Program counter
SIGNAL Next_Instruction:STD_LOGIC_VECTOR(2 DOWNTO 0);

--Adder 3 bit
SIGNAL THREE_BIT_ADDER_OUT:STD_LOGIC_VECTOR(2 DOWNTO 0);
SIGNAL C_OUTT:STD_LOGIC;

--Adder_Subtractor
SIGNAL M,OVERFLOW,ZERO,C_OUT:STD_LOGIC;

--Register Bank
SIGNAL R0,R1,R2,R3,R4,R5,R6,R7,Reg_Bank_In:STD_LOGIC_VECTOR(3 DOWNTO 0);
signal pushButton_temp : std_logic;

--instruction decoder
SIGNAL Reg_1,Reg_2,Reg_EN:STD_LOGIC_VECTOR(2 DOWNTO 0);
SIGNAL LS_temp:STD_LOGIC;
SIGNAL ASU_temp:STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL Immediatevalue_temp:STD_LOGIC_VECTOR(3 DOWNTO 0);

-----Decoder
SIGNAL Instruction: STD_LOGIC_VECTOR(11 DOWNTO 0);
SIGNAL JumpFlag:STD_LOGIC;
SIGNAL ATJ:STD_LOGIC_VECTOR(2 DOWNTO 0);

---ROM
SIGNAL memory_select:STD_LOGIC_VECTOR(2 DOWNTO 0);

-----MUX 8 4 bit
SIGNAL MUX_8_OUT0,MUX_8_OUT1:STD_LOGIC_VECTOR(3 DOWNTO 0);

begin

Program_Counter:ProgramCounter
  Port map(
    Reset=>pushButton_temp,
    Clk=>clk_temp,
    -- Clk=>clk_temp2,
    A=>Next_Instruction,
    memory_select=>memory_select

```

);

```
Reg_Bank_0:Reg_Bank  
  port map(  
    Clk=>clk_temp,  
    Reg_EN=>Reg_EN,  
    Reset=>pushButton_temp,  
    Reg_Bank_In=>Reg_Bank_In,  
    REG_0_OUT=>R0,  
    REG_1_OUT=>R1,  
    REG_2_OUT=>R2,  
    REG_3_OUT=>R3,  
    REG_4_OUT=>R4,  
    REG_5_OUT=>R5,  
    REG_6_OUT=>R6,  
    REG_7_OUT=>R7  
  );
```

```
MUX_2_3bit_0:MUX_2_3bit  
  port map(  
    A=>ATJ,  
    B=>THREE_BIT_ADDER_OUT,  
    S=>JumpFlag,  
    Q=>Next_Instruction  
  );
```

```
Instruction_Decoder:InstructionDecoder  
  Port map(  
    Instruction=>Instruction,  
    RCJ=>MUX_8_OUT0,  
    RegEn =>Reg_EN,  
    LS =>LS_temp,  
    Immediatevalue=>Immediatevalue_temp,  
    Reg_1=>Reg_1,  
    Reg_2 =>Reg_2,  
    Add_Sub_Select =>M,  
    JumpFlag=>JumpFlag,  
    ATJ=>ATJ  
  );
```

```
Adder_3bit_0:Adder_3bit  
  Port map(  
    A=>memory_select,  
    B => "001",  
    S=>THREE_BIT_ADDER_OUT,  
    C_out=>C_OUTT  
  );
```

```
MUX_8_4bit_0:MUX_8_4bit  
  port map(  
    Reg_Sel =>Reg_1,  
    R0 =>R0,
```

```

    R1 =>R1,
    R2 =>R2,
    R3 =>R3,
    R4 =>R4,
    R5 =>R5,
    R6 =>R6,
    R7 =>R7,
    Mux_Out =>MUX_8_OUT0
);
MUX_8_4bit_1:MUX_8_4bit
    port map(
        Reg_Sel =>Reg_2,
        R0 =>R0,
        R1 =>R1,
        R2 =>R2,
        R3 =>R3,
        R4 =>R4,
        R5 =>R5,
        R6 =>R6,
        R7 =>R7,
        Mux_Out =>MUX_8_OUT1
    );
MUX_2_4bit_0: MUX_2_4bit
    port map(
        A=>Immediatevalue_temp,
        B=>ASU_temp,
        Q=>Reg_Bank_In,
        S=>LS_temp
    );

Adder_Subtractor: Adder_Subtractor_4bit
    Port map (
        A =>MUX_8_OUT0,
        B =>MUX_8_OUT1,
        M =>M,
        S =>ASU_temp,
        C_OUT =>C_OUT,
        ZERO =>ZERO,
        OVERFLOW => OVERFLOW
    );

ROM_0 :ROM
    Port map(
        address=>memory_select,
        data=>Instruction
    );

Slow_Clk_0 :Slow_Clk
    Port map(
        Clk_in=>Clk,
        Clk_out=>clk_temp2
    );

```

```

clk_temp <= Clk;
nextInsVal <= Next_Instruction;
pushButton_temp <= pushButton;
LED<=R7;
LED_R6 <= R6;
LED_R5 <= R5;
LED_OVERFLOW<=OVERFLOW;
LED_ZERO<=ZERO;
RegisterEnable<=Reg_EN;
RegisterBank_DataIn<=Reg_Bank_In;
Imm_Value<=Immediatevalue_temp;
Instruction_temp <= Instruction;


```

end Behavioral;


Timing Diagrams

4-bit Adder/Subtractor


For addition

 


For subtraction

 


3 – bit Adder

 


Program Rom

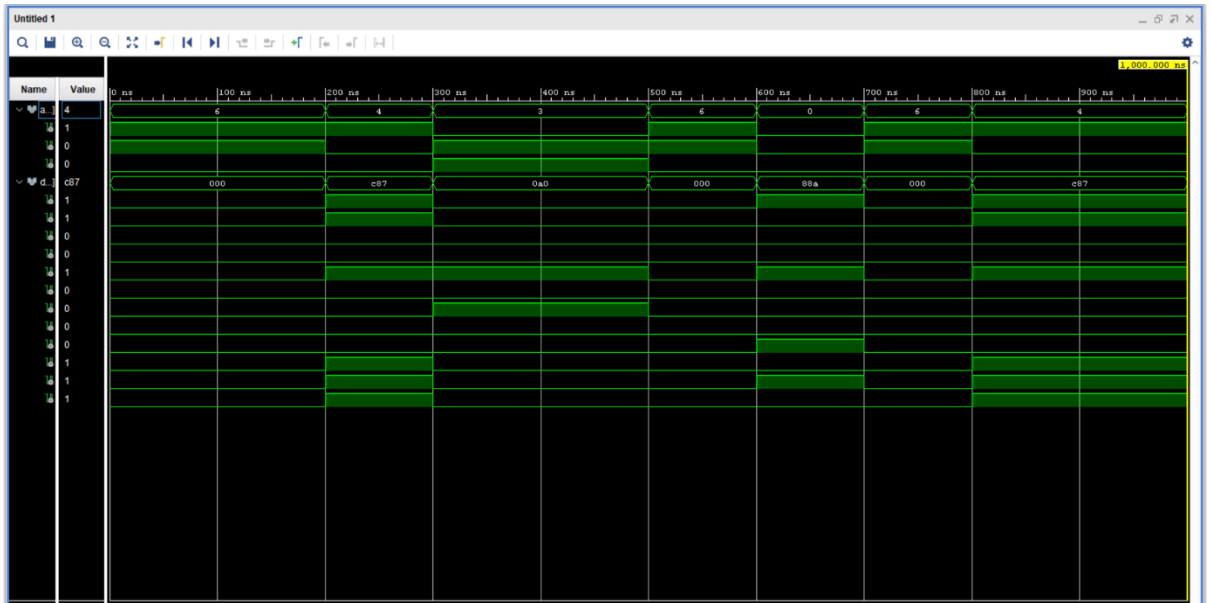


3 – bit Program Counter

 


MUX_2way_3-bit

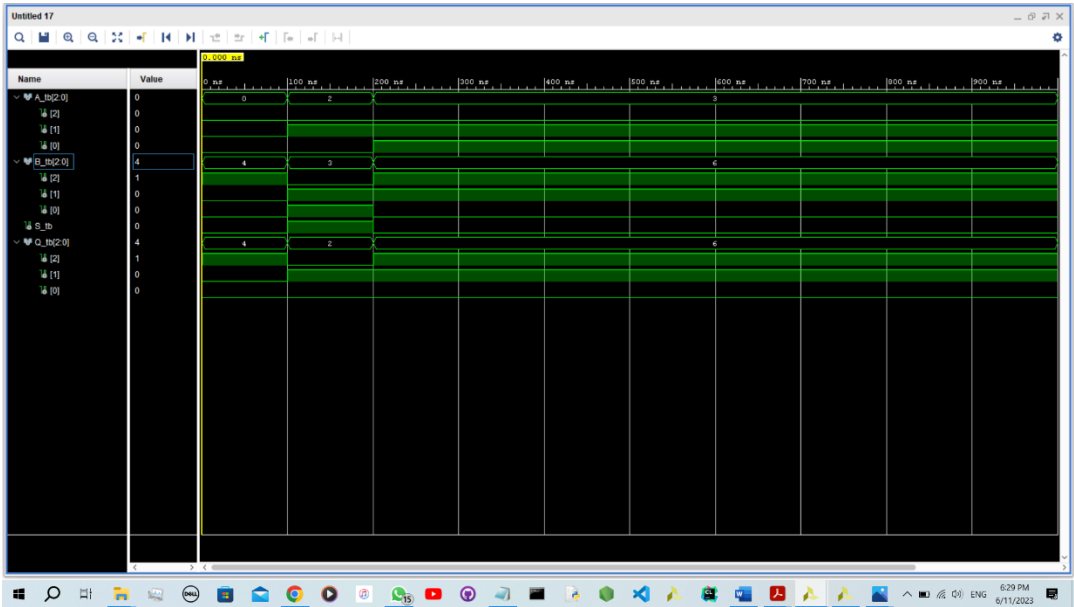


MUX_2way_4-bit

 


MUX_8way_4-bit

 


Register Bank

 

Instruction Decoder

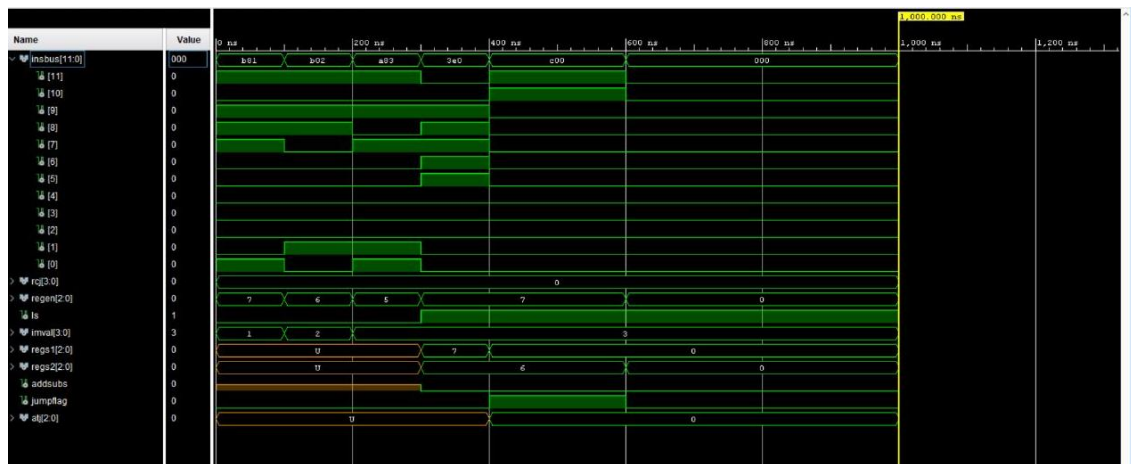

Nano Processor

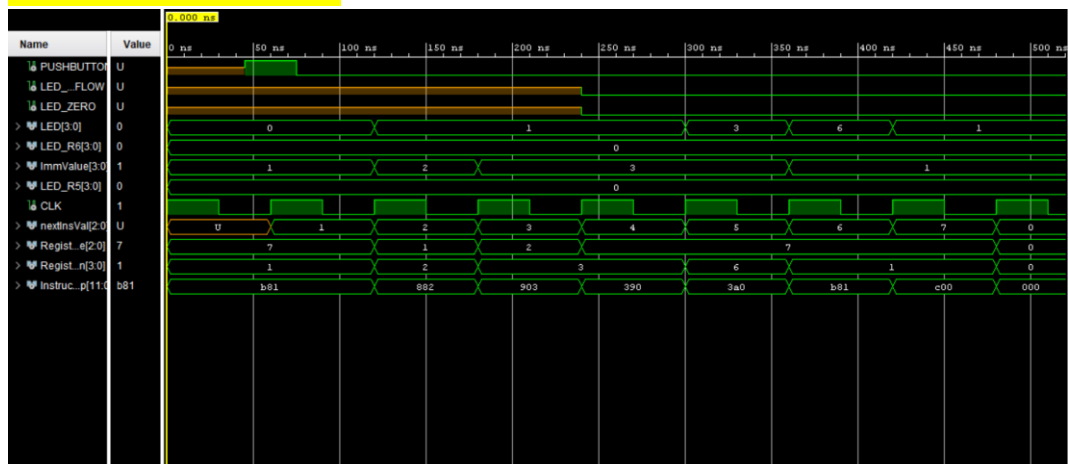

Conclusions from the Lab

In this lab, we designed and implemented essential components to create a functional nanoprocessor. These components included an add/subtract unit, adder, program counter, multiplexers, register bank, ROM, and instruction decoder. We successfully tested the processor by writing an Assembly program to calculate the total of integers from 1 to 3, converting it to machine code, and executing it on the development board. We faced challenges with component integration, timing, and module activation, but overcame them through efficient logic and thorough testing. The lab provided hands-on experience in computer organization, digital design, and teamwork skills, enhancing our understanding and appreciation for processor design.